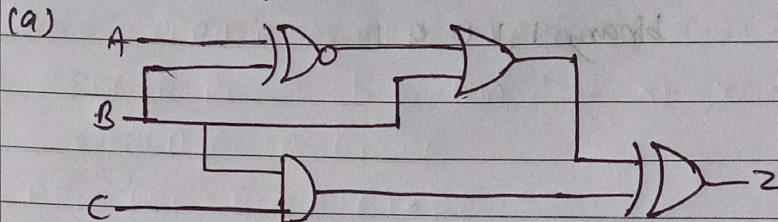


Assignment-2 Boolean Algebra

1) Derive the output expression 'z' for the below circuits and draw the simplified circuits.



→ From the circuit

• First Gate = XOR

$$(A \oplus B)' = AB + A'B'$$

• Second gate = OR

$$(A \oplus B)' + B$$

• Bottom Gate = AND

$$BC$$

• Final Gate = XOR

Output expression: $f = ((A \oplus B)' + B) \oplus (BC)$

Simplify:

$$(A \oplus B)' = AB + A'B'$$

$$AB + B = B(A + 1) = B$$


$$AB + A'B' + B = B + A'B' = B + A'$$

$$B + A'B' = (A' + B)(B + B')$$


$$= \underline{A' + B}$$

∴ Simplified Expression:

$$f = (A' + B) \oplus BC$$

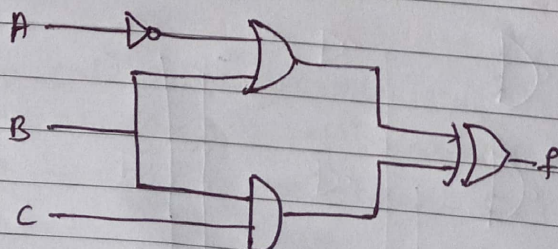

(b)

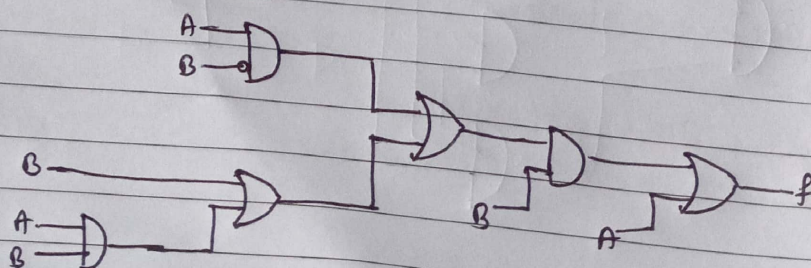

→ from the circuit,

• TOP AND = AB'

• Bottom AND: AB

• First OR: $B + AB = B$

• Second OR: $AB' + B = A + B$

• AND with B:

$$(A+B)B = AB + BB = AB + B = B(A+1) = B$$


• last OR:

$$B + A = A + B$$


output expression: $f = [(AB') + (B + AB)]B + A$

simplified expression:

$$f = A + B$$

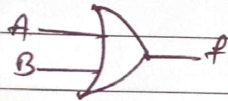

(c)

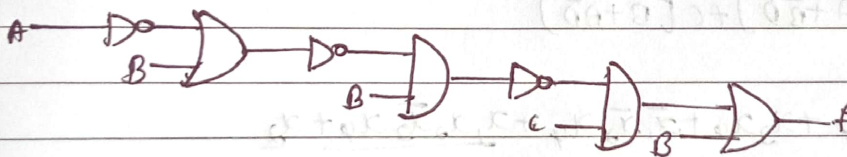

→ from the circuit

• NOT on A: $\bar{A}$

• OR: $\bar{A} + B$

• NOT: $\overline{(\bar{A} + B)} = \bar{\bar{A}} \bar{B} = AB$

• AND: $AB \cdot B = 0$

• NOT: $\bar{0} = 1$

• AND: $1 \cdot C = C$

• OR: $B + C$

O/P expression: $f = [C(\bar{A} + B)B] + B$

$$f = [C(\bar{A} + B)'B] + B$$

simplified expression

$$f = B + C$$



2] minimize the following Boolean expressions using Boolean postulates.

(a) $\bar{A}\bar{C}\bar{D}E + \bar{A}\bar{B}\bar{D} + ABCE + ABD$

→ $\bar{A}\bar{D}(CE + \bar{B}) + AB(CE + D)$

(b) $\bar{A}\bar{B}\bar{C} + ABD + \bar{A}C + \bar{A}C\bar{D} + A\bar{C}D + A\bar{B}\bar{C}$

→ $\bar{A}C + \bar{A}C\bar{D} = \bar{A}C$ absorption law: $x + xy = x$

$\bar{A}\bar{B}\bar{C} + ABD + \bar{A}C + \bar{A}C\bar{D} + A\bar{B}\bar{C}$

$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} = \bar{B}\bar{C}(\bar{A} + A) = \bar{B}\bar{C}$

$\bar{B}\bar{C} + ABD + \bar{A}C + A\bar{C}D$

$ABD + \bar{A}C + \bar{C}(\bar{B} + AD)$

(c) $\bar{A}\bar{C} + BC + \bar{A}\bar{B} + \bar{A}BC + AC\bar{D} + \bar{B}\bar{C}\bar{D}$

→ $\bar{A}BC + BC = BC$ absorption law: $x + xy = x$

$\bar{A}\bar{C} + BC + \bar{A}\bar{B} + AC\bar{D} + \bar{B}\bar{C}\bar{D}$

$\bar{C}[\bar{A} + \bar{B}\bar{D}] + BC + \bar{A}\bar{B} + AC\bar{D}$

$\bar{A}\bar{B} + \bar{C}[\bar{A} + \bar{B}\bar{D}] + C[B + A\bar{D}]$


(d) $\bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4 + x_2$

$x_2 + x_1x_2\bar{x}_3x_4 = x_2$ absorption law: $x + xy = x$

$\bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_2$

$x_1[\bar{x}_3\bar{x}_4 + \bar{x}_2x_4] + x_3x_4 + x_2$

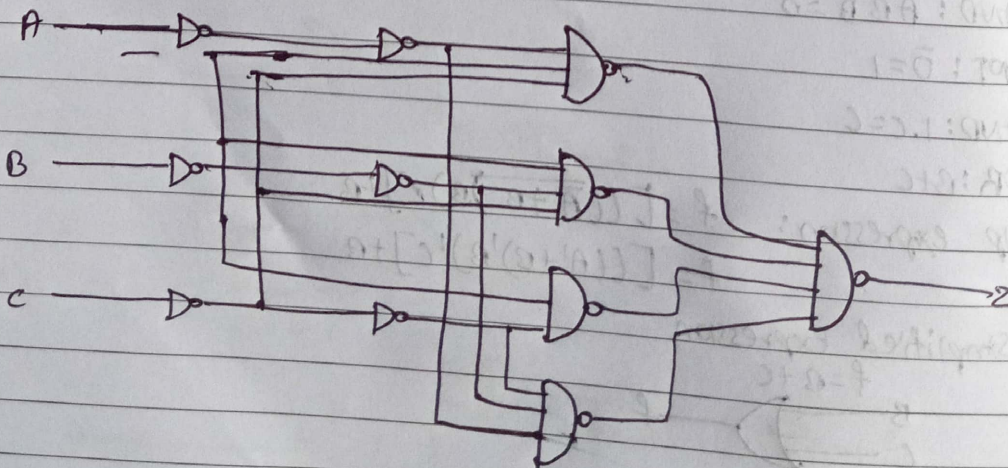3] which single gate can represent the functionality of given circuit?



→ The first 4 Nand gates give 4 minterms corresponding to the cases where an odd number of inputs are 1.

$$\bar{A}\bar{B}C, \bar{A}B\bar{C}, A\bar{B}\bar{C}, A\bar{B}C$$

The final Nand combines these o/p's giving

$$Z = \bar{P}_1, \bar{P}_2, \bar{P}_3, \bar{P}_4 = P_1 + P_2 + P_3 + P_4$$


$$Z = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

This is exactly the boolean expression for a 3-input exclusive-OR-(XOR) gate:

$$Z = A \oplus B \oplus C$$

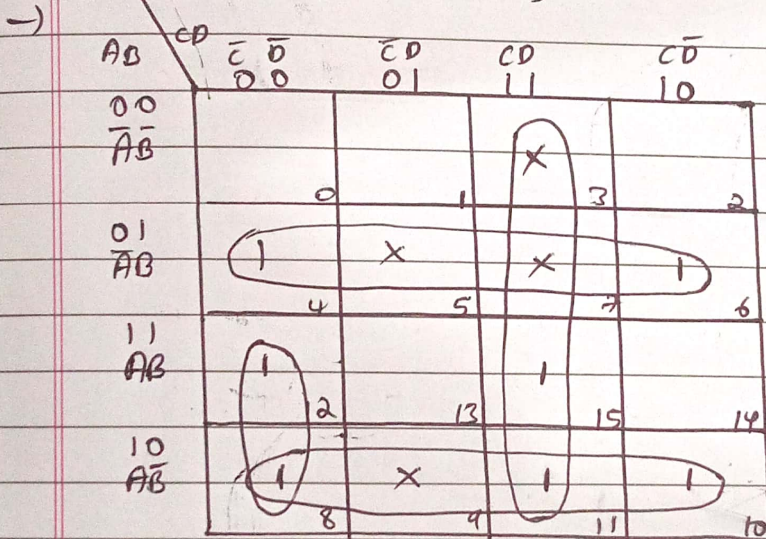
4) minimize the following Boolean expressions using K-map

$$(a) f(a, b, c, d) = \sum m(4, 6, 8, 10, 11, 12, 15) + \sum d(3, 5, 7, 9)$$



$$\therefore f = \bar{A}B + A\bar{B} + CD + A\bar{C}\bar{D}$$
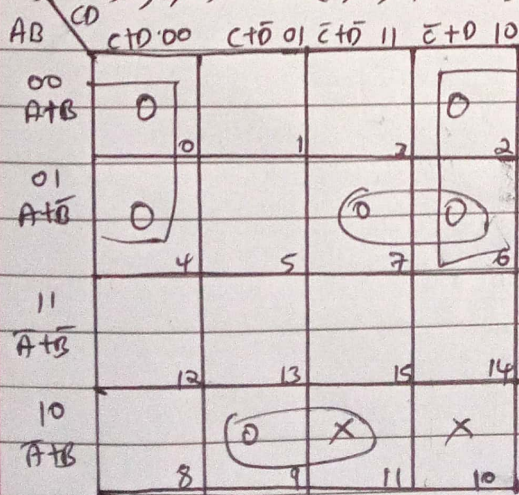
$$(b) f(a, b, c, d) = \pi M(0, 2, 4, 6, 7, 9) + \pi D(10, 11)$$



$$\therefore f = (A + D)(A + B + \bar{C})(\bar{A} + B + \bar{D})$$